


RESISTORS IN SERIES AND PARALEL CONNECTION

by Cecil Sie

Note :

1. Two resistors are in series when
 - they are connected with only one hand
 - the connection between the two resistors is not connected to any other object.
2. Two resistors are in paralel when :
 - they are connected with two hands.

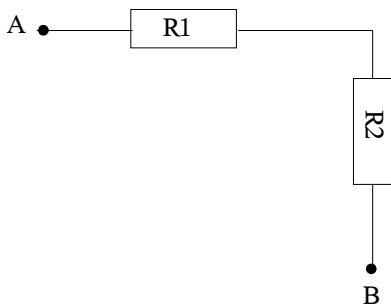(1) R_1 and R_2 are combined to form R_{AB} .




Are R_1 and R_2 connected by one hand only ?

_____ .

Is the connection between R_1 and R_2 connected to other object ? _____ .

Are R_1 and R_2 connected in series ? _____ .

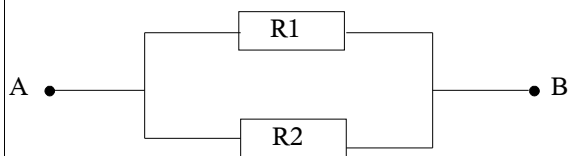(2) R_1 and R_2 are combined to form R_{AB} .




Are R_1 and R_2 connected by two hands ?

_____ .

Are R_1 and R_2 connected in paralel ? _____ .

Call 90885633 to have Maths, Physics and Chemistry tuition.

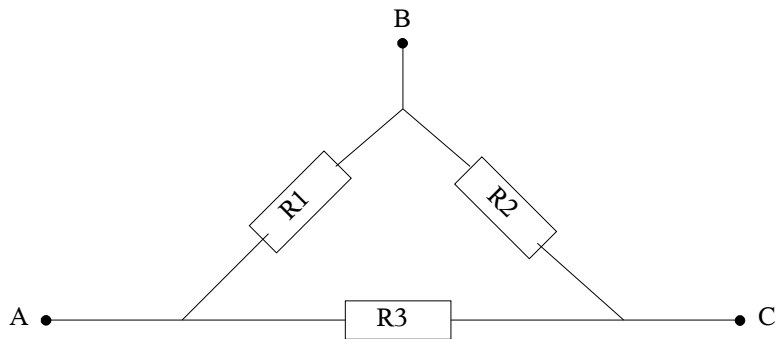(3) R_1 , R_2 and R_3 are combined to form R_{AC} .



Are R_1 and R_3 connected by one hand only ? _____ .
 Is the connection between R_1 and R_3 connected to other object ? _____ .
 What is the object ? _____ .
 Are R_1 and R_3 connected in series ? _____ .
 Are R_1 and R_3 connected by two hands ? _____ .
 Are R_1 and R_3 connected in parallel ? _____ .

Are R_2 and R_3 connected by one hand only ? _____ .
 Is the connection between R_2 and R_3 connected to other object ? _____ .
 What is the object ? _____ .
 Are R_2 and R_3 connected in series ? _____ .
 Are R_2 and R_3 connected by two hands ? _____ .
 Are R_2 and R_3 connected in parallel ? _____ .

Are R_1 and R_2 connected by two hands ? _____ .
 Are R_1 and R_2 connected in parallel ? _____ .
 Are R_1 and R_2 connected by one hand only ? _____ .
 Is the connection between R_1 and R_2 connected to other object ? _____ .
 Why “point B is not considered as “other object” ? _____ .
 Are R_1 and R_2 connected in series ? _____ .

Download this exercises from www.singaporestudent.com

Note :


1. Formula to combine resistors connected in series :

$$R_1 + R_2 = R_{12}$$

2. Formula to combine resistors connected in parallel :

$$R_{12} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

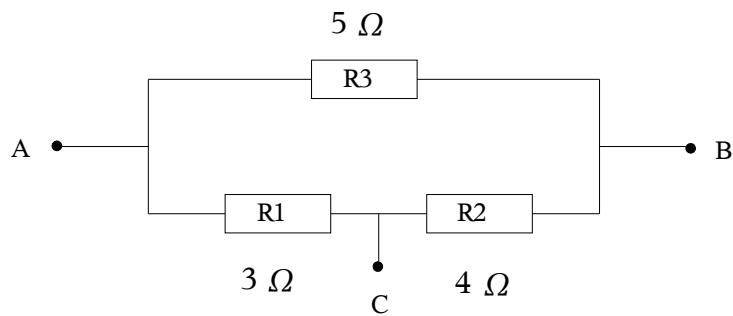(4) R_1 , R_2 and R_3 are combined to produce R_{AB} .



Are R_1 and R_2 connected by two hands ? _____ .

Are R_1 and R_2 connected in parallel ? _____ .

Are R_1 and R_2 connected by one hand only ? _____ .


Is the connection between R_2 and R_3 connected to other object ? _____ .

Why "point C" is not considered as "other object" ? _____ .

Are R_1 and R_2 connected in series ? _____ .


$R_{12} =$ _____ Ω .

Physics is fun

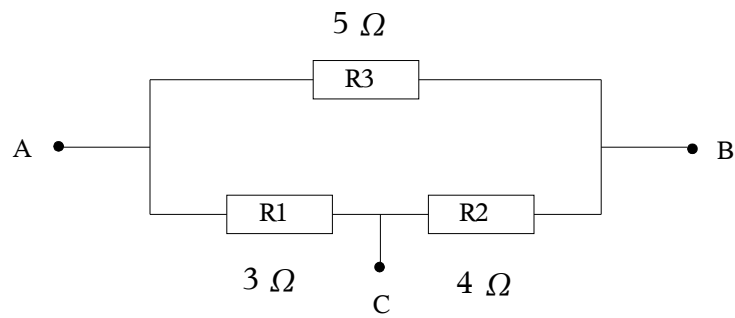


When the above diagram is redrawn with R_1 and R_2 combined, the result is :


(a)

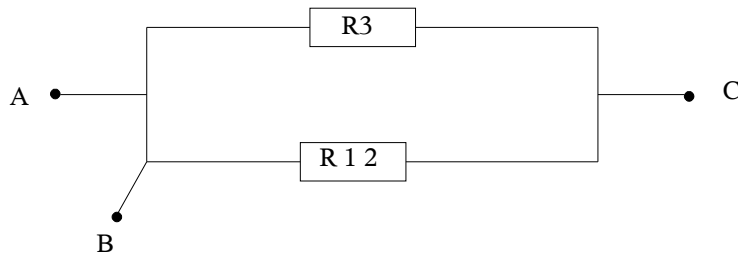


(b)

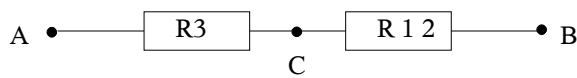


(c)

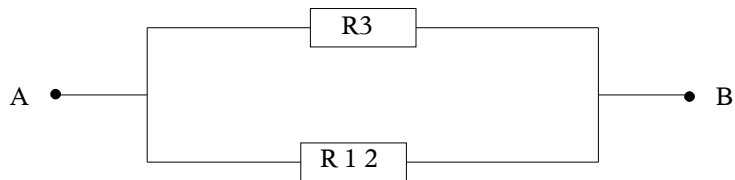

(d)

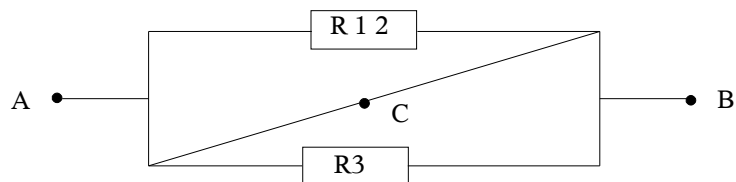

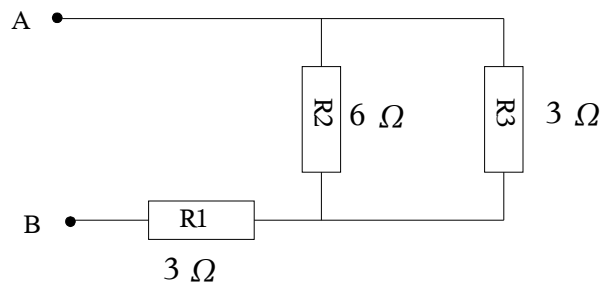(5) R_1 , R_2 and R_3 are combined to produce R_{AB} .







(a) Are R_1 and R_2 connected by one hand only ? _____ .
 Is the connection between R_1 and R_2 connected to other object ? _____ .
 What is the object ? _____ .
 Are R_1 and R_2 connected in series ? _____ .
 Are R_1 and R_2 connected by two hands ? _____ .
 Are R_1 and R_2 connected in paralel ? _____ .
 Can you combine R_1 and R_2 to become R_{12} ? _____ .
 Why ? _____ .

(b) Are R_1 and R_3 connected by one hand only ? _____ .
 Is the connection between R_1 and R_3 connected to other object ? _____ .
 What is the object ? _____ .
 Are R_1 and R_3 connected in series ? _____ .
 Are R_1 and R_3 connected by two hands ? _____ .
 Are R_1 and R_3 connected in paralel ? _____ .
 Can you combine R_1 and R_3 to become R_{13} ? _____ .
 Why ? _____ .

(c) Are R_2 and R_3 in series ? _____ .
 Are R_2 and R_3 in paralel ? _____ .
 $R_{23} =$ _____ Ω

Call 90885633 to have Maths, Physics and Chemistry tuition.

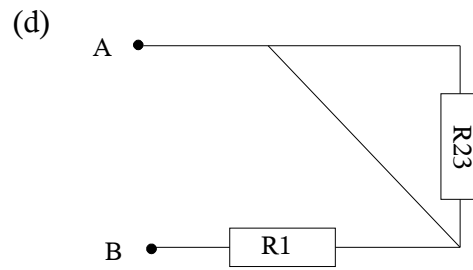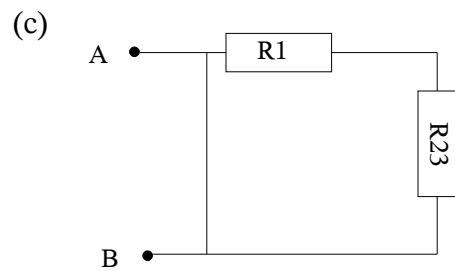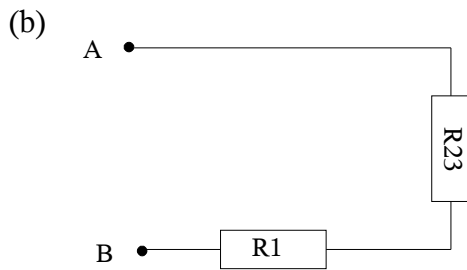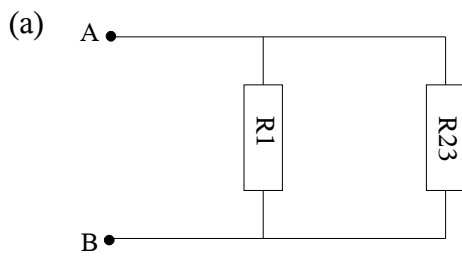
(d) When the above diagram is redrawn with R_1 and R_2 combined, the result is :



(e) Are R_{23} and R_1 in series ? _____ .
 Are R_{23} and R_1 in paralel ? _____ .
 $R_{123} = \text{_____ } \Omega$

Study everyday and get A on Physics.

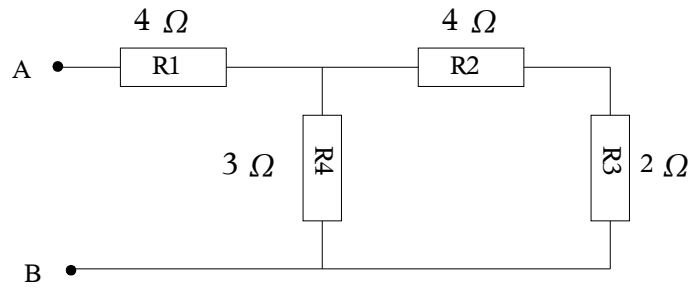(6) R_1 , R_2 , R_3 and R_4 are combined to produce R_{AB} .







(a) Are R_1 and R_2 in series? _____ .
 Are R_1 and R_2 in parallel? _____ .
 Can you combine R_1 and R_2 to become R_{12} ? _____ .

(b) Are R_1 and R_4 in series? _____ .
 Are R_1 and R_4 in parallel? _____ .
 Can you combine R_1 and R_4 to become R_{14} ? _____ .

(c) Are R_2 and R_3 in series? _____ .
 Are R_2 and R_3 in parallel? _____ .
 Can you combine R_2 and R_3 to become R_{23} ? _____ .
 $R_{23} =$ _____ Ω

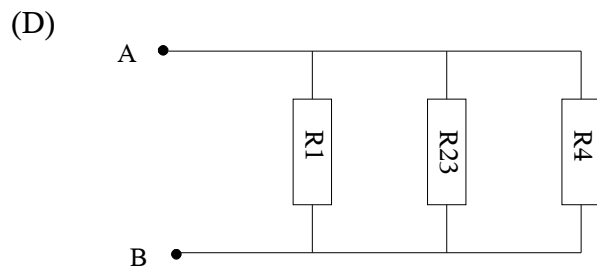
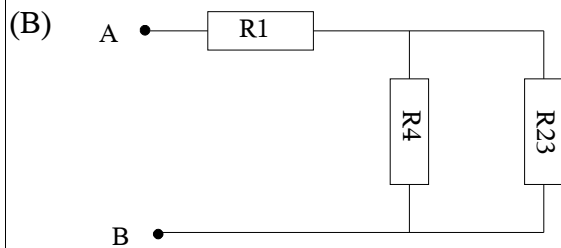
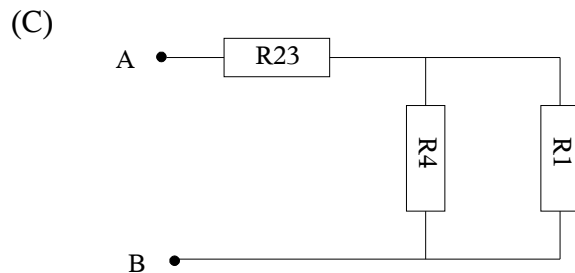
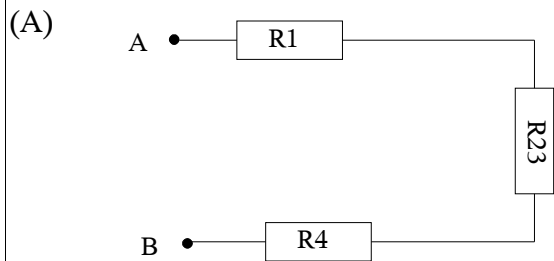
(d) When the above diagram is redrawn with R_2 and R_3 combined, the result is :



(e) Are R_1 and R_{23} in series ? _____ .
 Are R_1 and R_{23} in paralel ? _____ .
 Can you combine R_1 and R_{23} to become R_{123} ? _____ .

(f) Are R_{23} and R_4 in series ? _____ .
 Are R_{23} and R_4 in paralel ? _____ .
 Can you combine R_{23} and R_4 to become R_{234} ? _____ .
 $R_{234} =$ _____ Ω

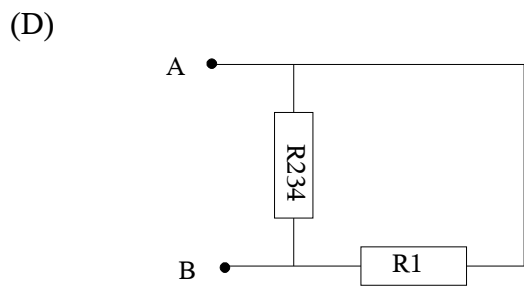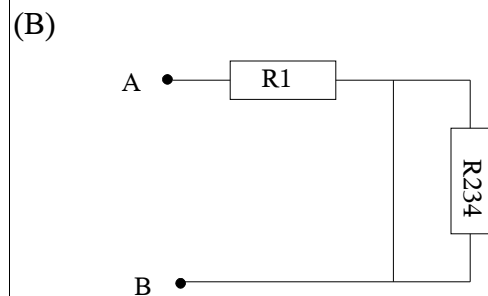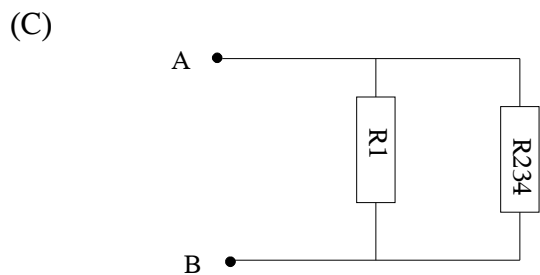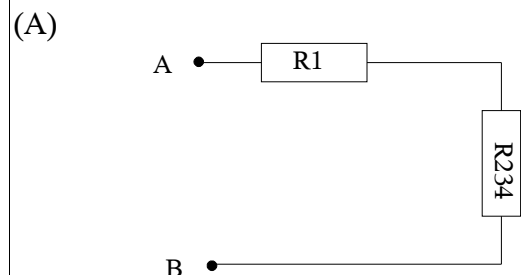
(g) When the above diagram is redrawn with R_{23} and R_4 combined, the result is :



(h) Are R_1 and R_{234} in series ? _____ .
 Are R_1 and R_{234} in paralel ? _____ .
 Can you combine R_1 and R_{234} to become R_{1234} ? _____ .
 $R_{1234} =$ _____ Ω
 $R_{AB} =$ _____ Ω

Download more physics exercises from www.singaporestudent.com

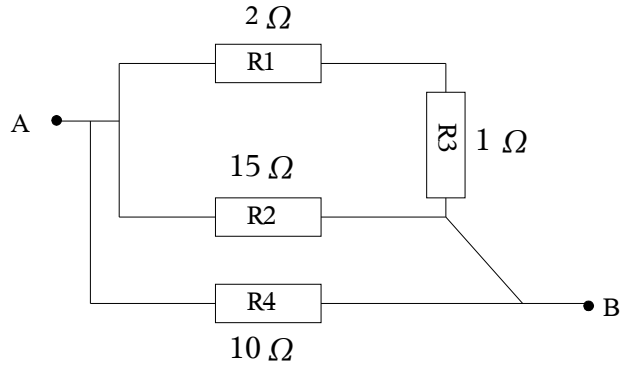(7) R_1 , R_2 , R_3 and R_4 are combined to produce R_{AB} .



(a) Are R_1 and R_2 in series? _____ .
 Are R_1 and R_2 in parallel? _____ .
 Can you combine R_1 and R_2 to become R_{12} ? _____ .

(b) Are R_3 and R_4 in series? _____ .
 Are R_3 and R_4 in parallel? _____ .
 Can you combine R_3 and R_4 to become R_{34} ? _____ .


(c) Are R_1 and R_3 in series? _____ .
 Are R_1 and R_3 in parallel? _____ .
 Can you combine R_1 and R_3 to become R_{13} ? _____ .
 $R_{13} =$ _____ Ω

(d) Redraw the above diagram with R_1 and R_3 combined as R_{13} !



(e) Are R_2 and R_4 in series? _____ .
 Are R_2 and R_4 in parallel? _____ .
 Are R_2 and R_{13} in parallel? _____ .
 Are R_2 , R_{13} and R_4 in parallel? _____ .
 $R_{1234} =$ _____ Ω
 $R_{AB} =$ _____ Ω

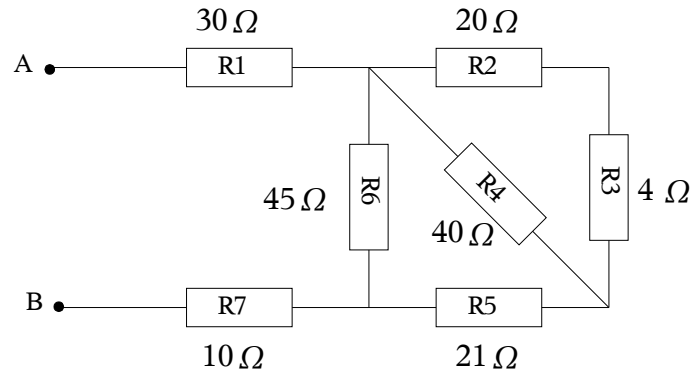(8) $R_1, R_2, R_3, R_4, R_5, R_6,$ and R_7 are combined to produce R_{AB} .




(a) Can you calculate R_{12} ? _____ .

Can you calculate R_{25} ? _____ .

Can you calculate R_{23} ? _____ .

$R_{23} =$ _____ Ω

 Redraw the above diagram with R_2 and R_3 combined as R_{23} !



(b) Can you calculate R_{123} ? _____ .

Can you calculate R_{235} ? _____ .

Can you calculate R_{234} ? _____ .

$R_{234} =$ _____ Ω

Redraw the above diagram with R_2 and R_4 combined as R_{234} !



Physics is fun.


(c) Can you calculate R_{1234} ? _____ .

Can you calculate R_{2346} ? _____ .

Can you calculate R_{2345} ? _____ .

$R_{2345} =$ _____ Ω

 Redraw the above diagram with R_{234} and R_5 combined as R_{2345} !



(d) Can you calculate R_{12345} ? _____ .

Can you calculate R_{23457} ? _____ .

Can you calculate R_{23456} ? _____ .

$R_{23456} =$ _____ Ω

Redraw the above diagram with R_{2345} and R_6 combined as R_{23456} !




(e) $R_{123456} =$ _____ Ω

$R_{1234567} =$ _____ Ω

$R_{AB} =$ _____ Ω

Subscribe to singaporestudent.com newsletter to get more of these exercises.

(9)

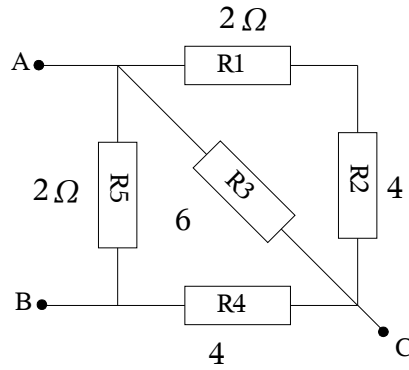

When R_1 , R_2 , R_3 , R_4 , and R_5 are combined to produce R_{AB} :

$$R_{12} = \underline{\hspace{2cm}} \Omega$$

$$R_{123} = \underline{\hspace{2cm}} \Omega$$

$$R_{1234} = \underline{\hspace{2cm}} \Omega$$

$$R_{12345} = \underline{\hspace{2cm}} \Omega$$

$$R_{AB} = \underline{\hspace{2cm}} \Omega$$

When R_1 , R_2 , R_3 , R_4 , and R_5 are combined to produce R_{AC} :

$$R_{12} = \underline{\hspace{2cm}} \Omega$$

$$R_{45} = \underline{\hspace{2cm}} \Omega$$

$$R_{12345} = \underline{\hspace{2cm}} \Omega$$

$$R_{AC} = \underline{\hspace{2cm}} \Omega$$

Why R_{AB} is not equal to R_{AC} . ? _____ .

Call 90885633 to have Maths, Physics and Chemistry tuition.